


Chapter 25: Circuit theory

Thursday October 6th

- Series/parallel circuits - finish examples from Tuesday
 - Complex circuit
 - Parallel batteries with internal resistance
- RC circuits
 - Charging a capacitor
 - Discharging a capacitor
 - Demonstration

Reading: up to page 431 in the text book (Ch. 25)


Example: multiple batteries

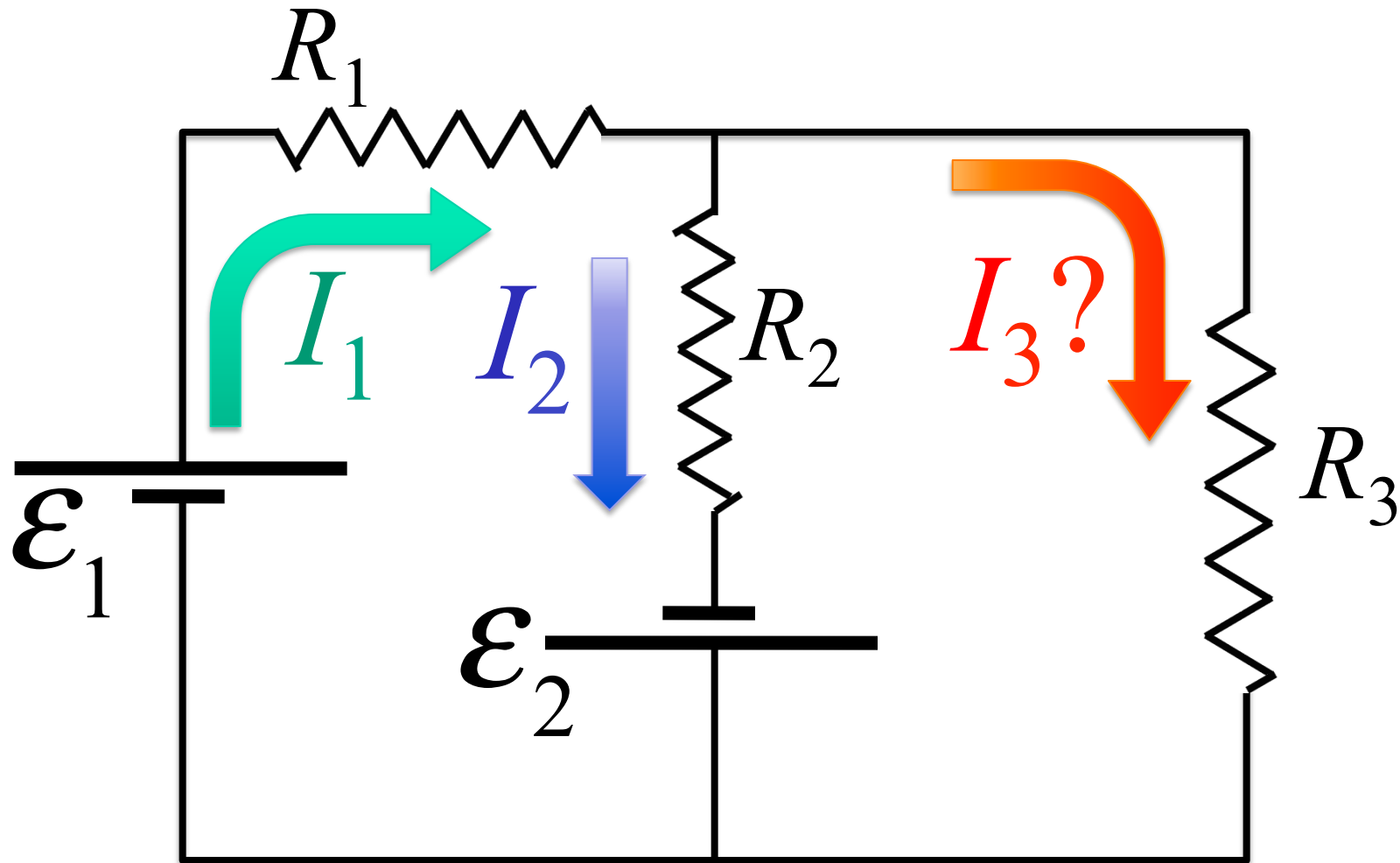

Find current I_3

$$\mathcal{E}_1 = 10 \text{ V}; \quad \mathcal{E}_2 = 20 \text{ V}; \quad R_1 = 15 \text{ } \Omega; \quad R_2 = 6 \text{ } \Omega; \quad R_3 = 7 \text{ } \Omega.$$


Example: multiple batteries

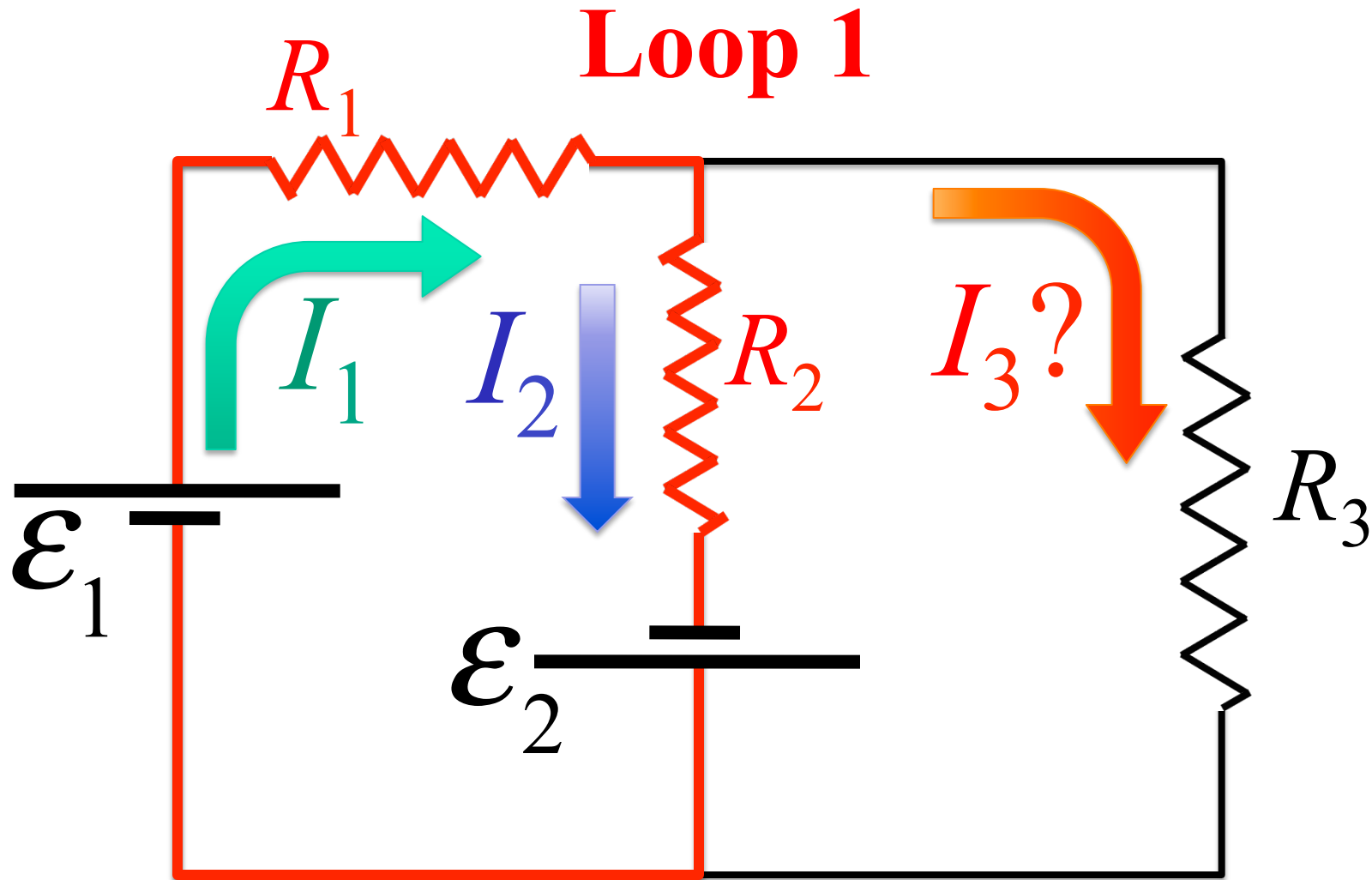

Find current I_3

$$\mathcal{E}_1 = 10 \text{ V}; \quad \mathcal{E}_2 = 20 \text{ V}; \quad R_1 = 15 \text{ } \Omega; \quad R_2 = 6 \text{ } \Omega; \quad R_3 = 7 \text{ } \Omega.$$

Example: multiple batteries

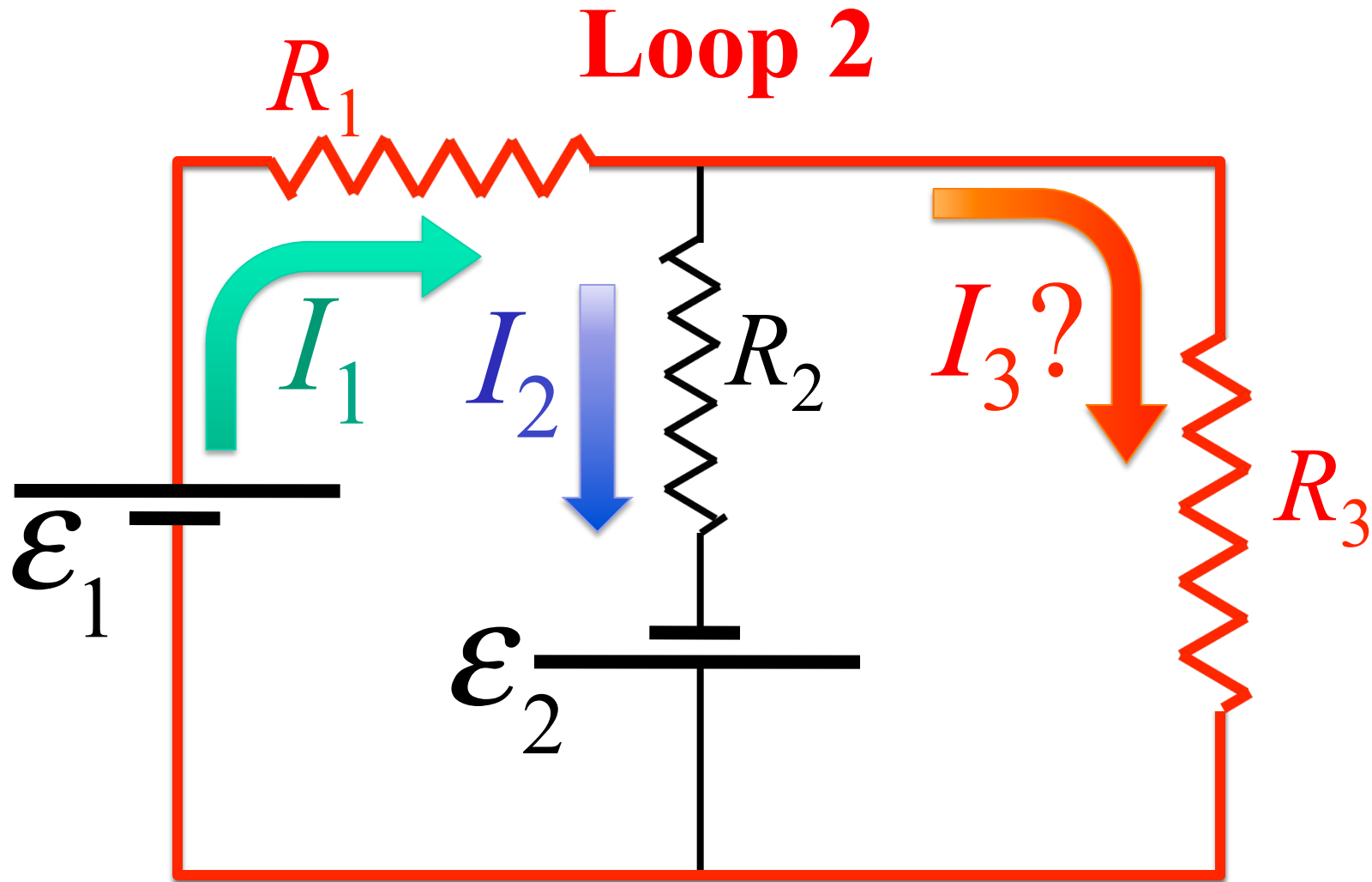


Find current I_3

$$\mathcal{E}_1 = 10 \text{ V}; \quad \mathcal{E}_2 = 20 \text{ V}; \quad R_1 = 15 \text{ } \Omega; \quad R_2 = 6 \text{ } \Omega; \quad R_3 = 7 \text{ } \Omega.$$

Example: multiple batteries


Loop 3

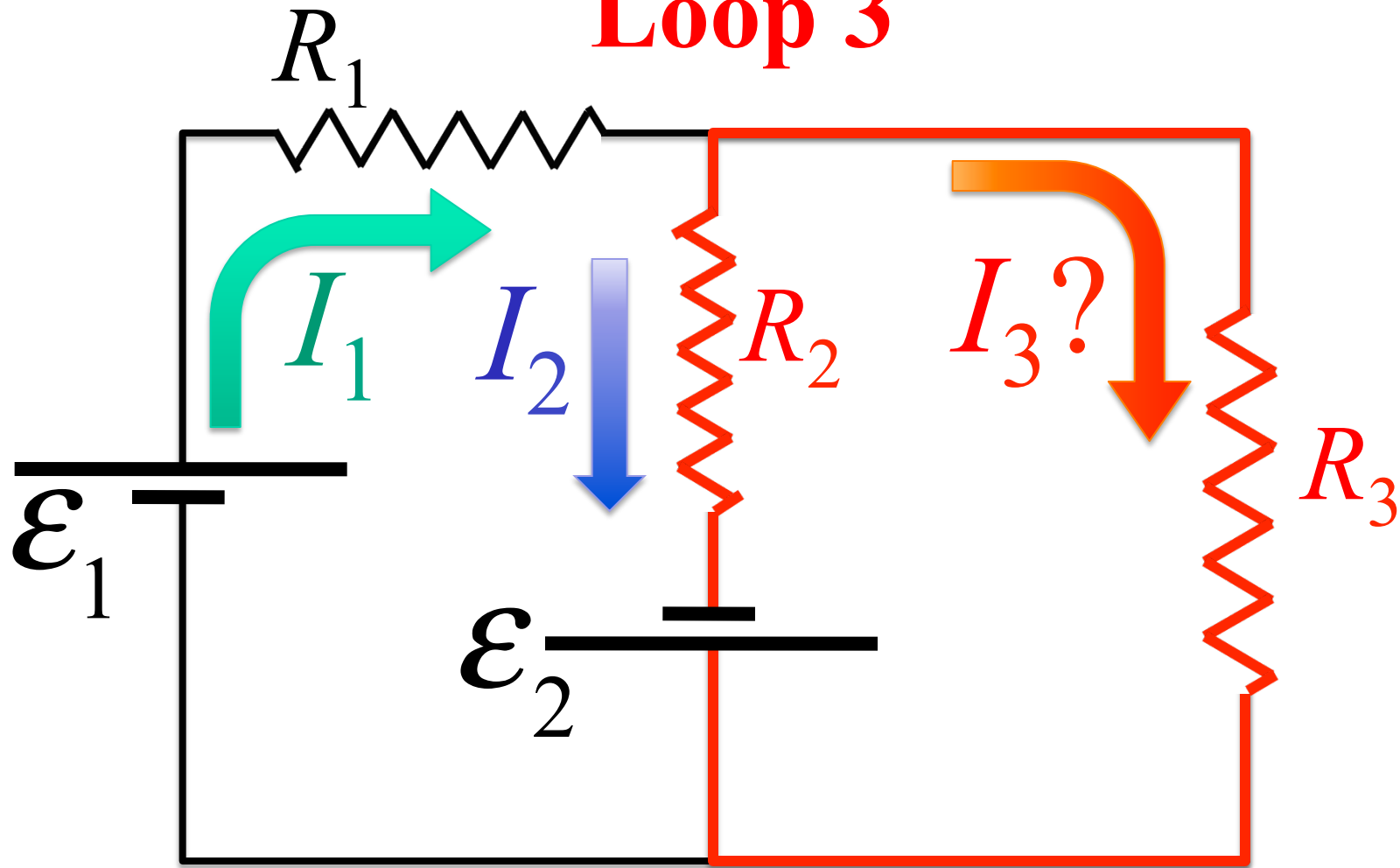


Find current I_3

$$\mathcal{E}_1 = 10 \text{ V}; \quad \mathcal{E}_2 = 20 \text{ V}; \quad R_1 = 15 \text{ } \Omega; \quad R_2 = 6 \text{ } \Omega; \quad R_3 = 7 \text{ } \Omega.$$

Example: parallel batteries

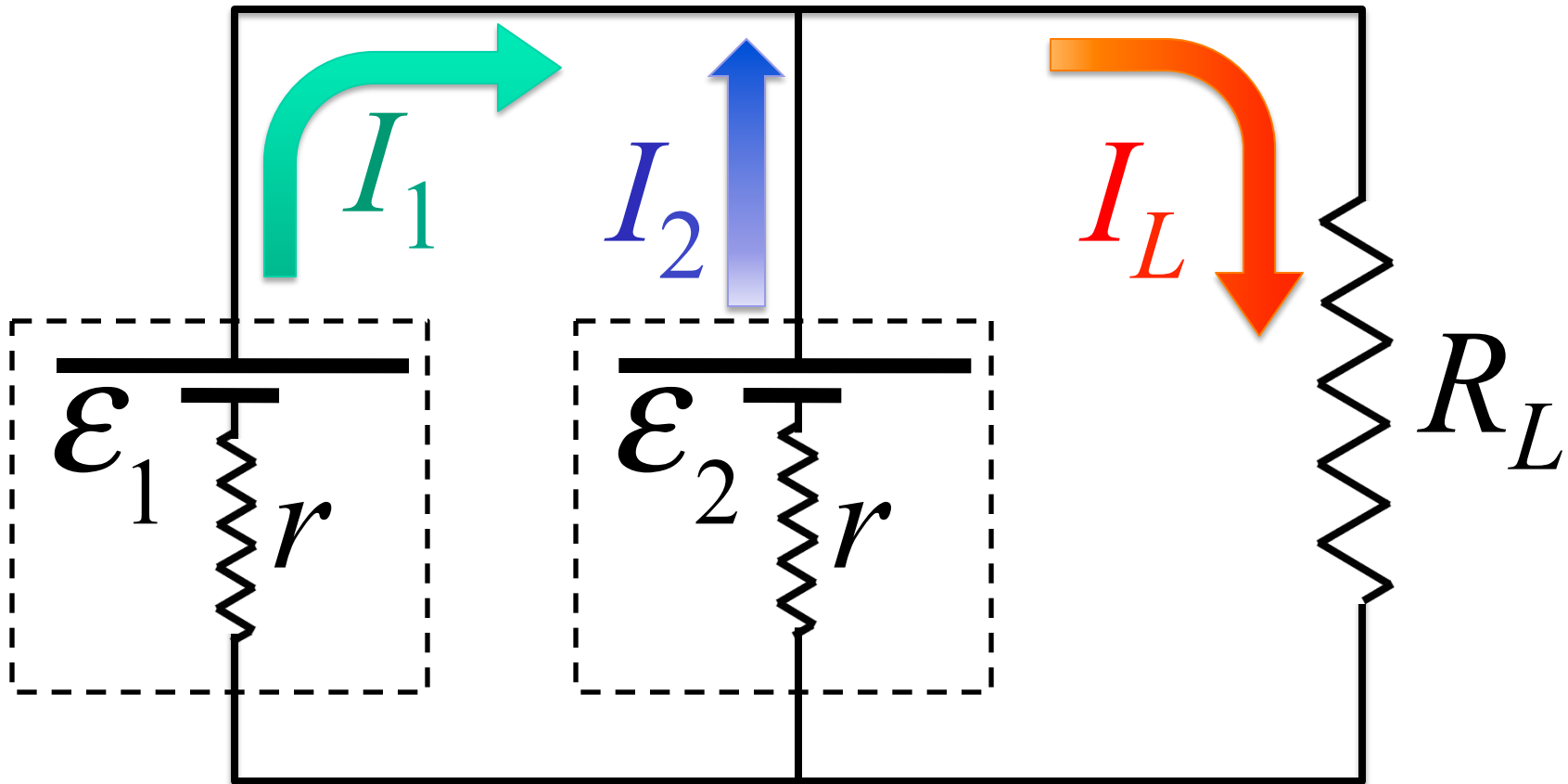


Example: parallel batteries

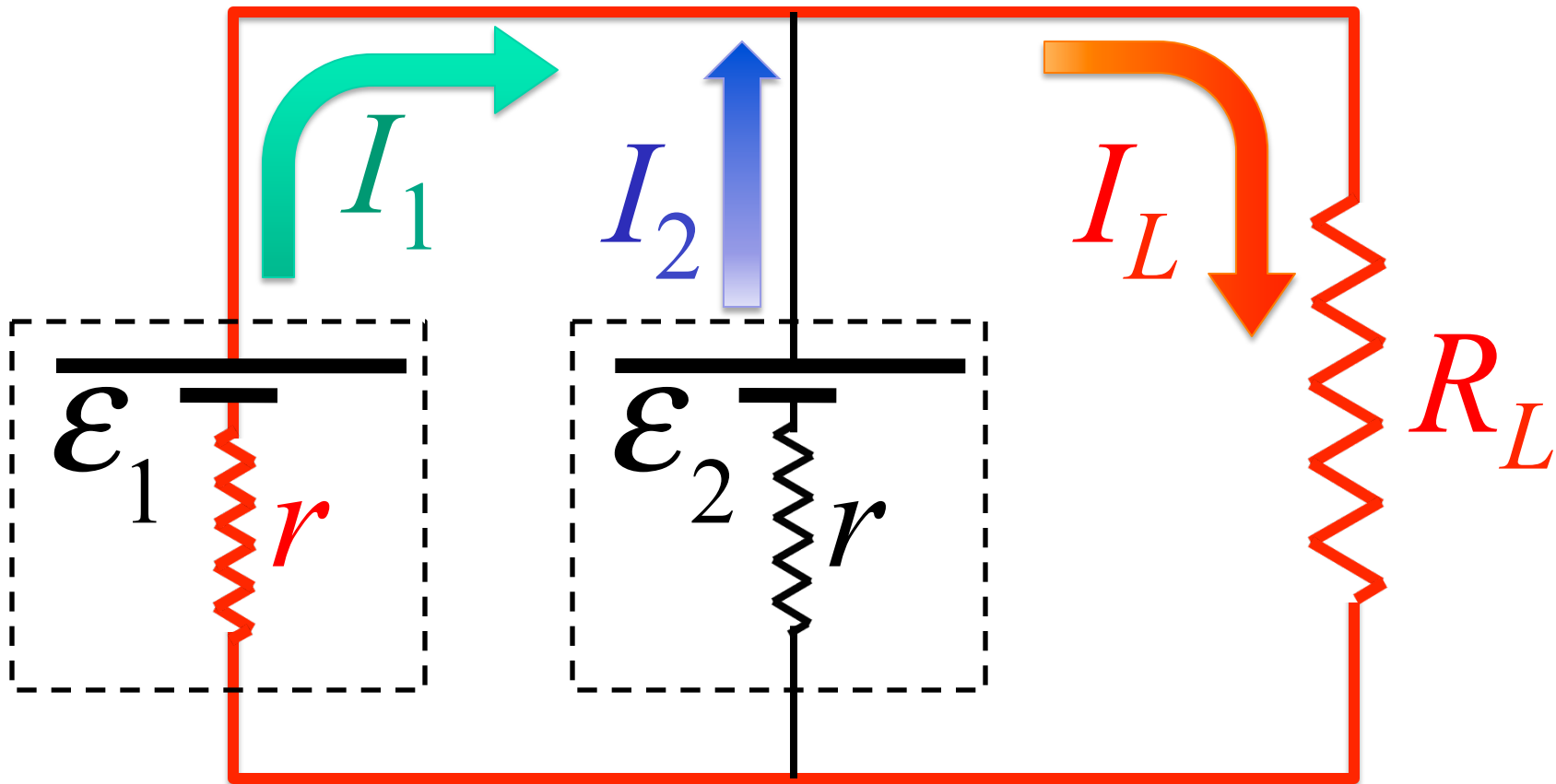


Loop 1

Example: parallel batteries

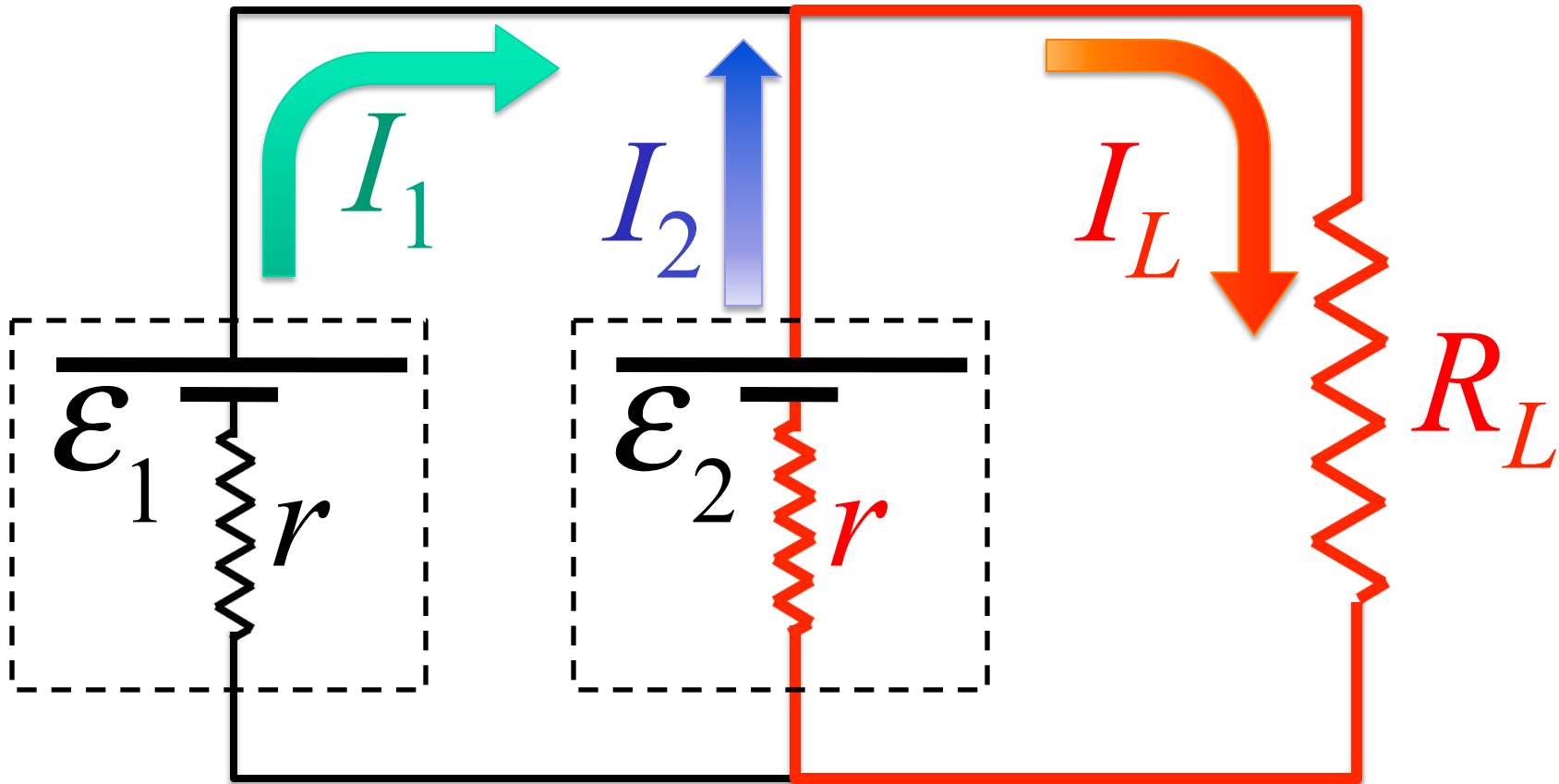

Loop 2

Example: parallel batteries

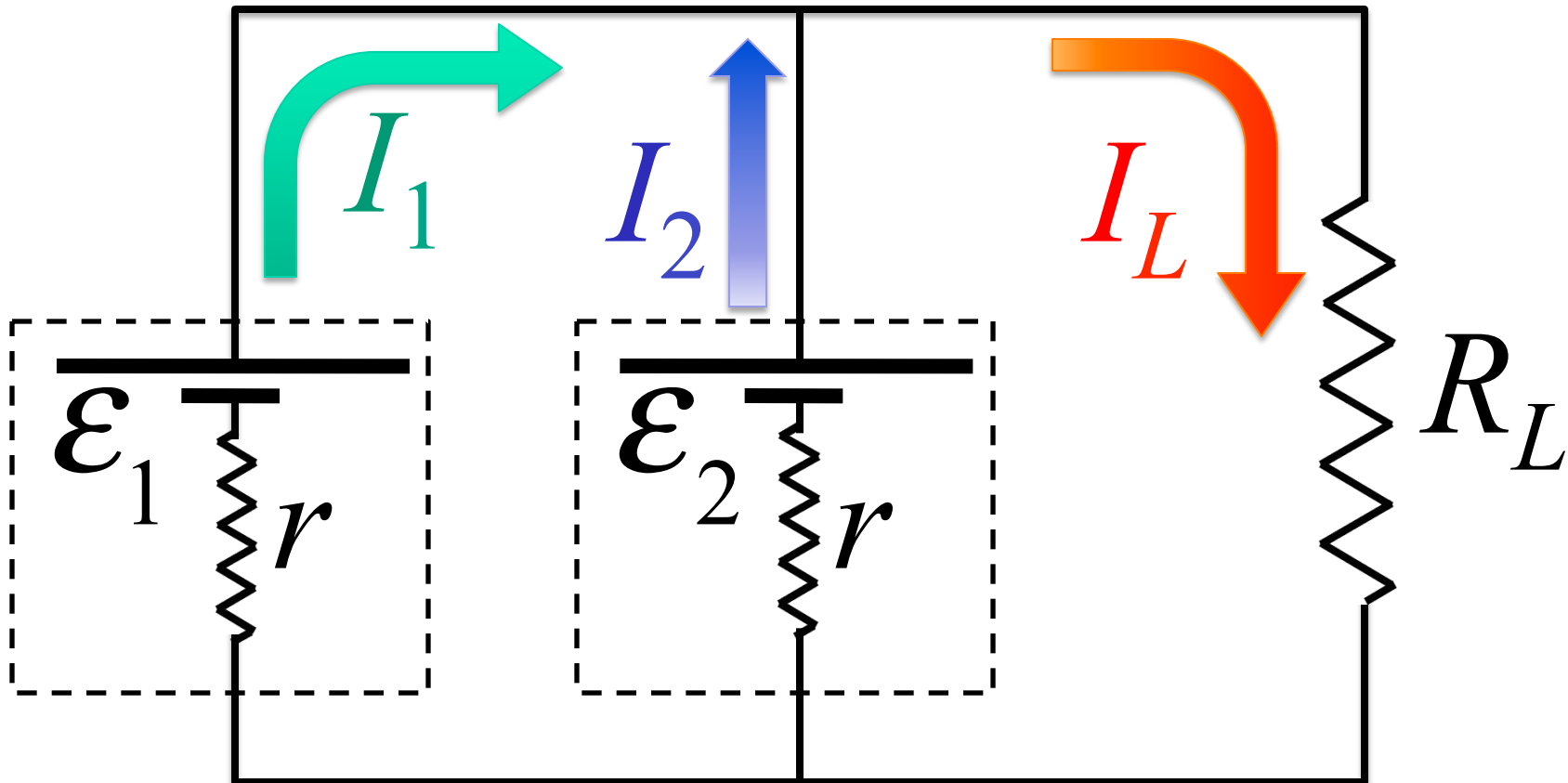


$$I_L = \frac{\mathcal{E}_1 + \mathcal{E}_2}{2R_L + r}, \text{ if } \mathcal{E}_1 = \mathcal{E}_2 = \mathcal{E}, \text{ then } I_L = \frac{2\mathcal{E}}{2R_L + r} = \frac{\mathcal{E}}{R_L + r/2}$$

Lesson: if you need lots of current, use batteries in parallel.

RC circuits (charging a capacitor)

Switch at a at $t = 0$

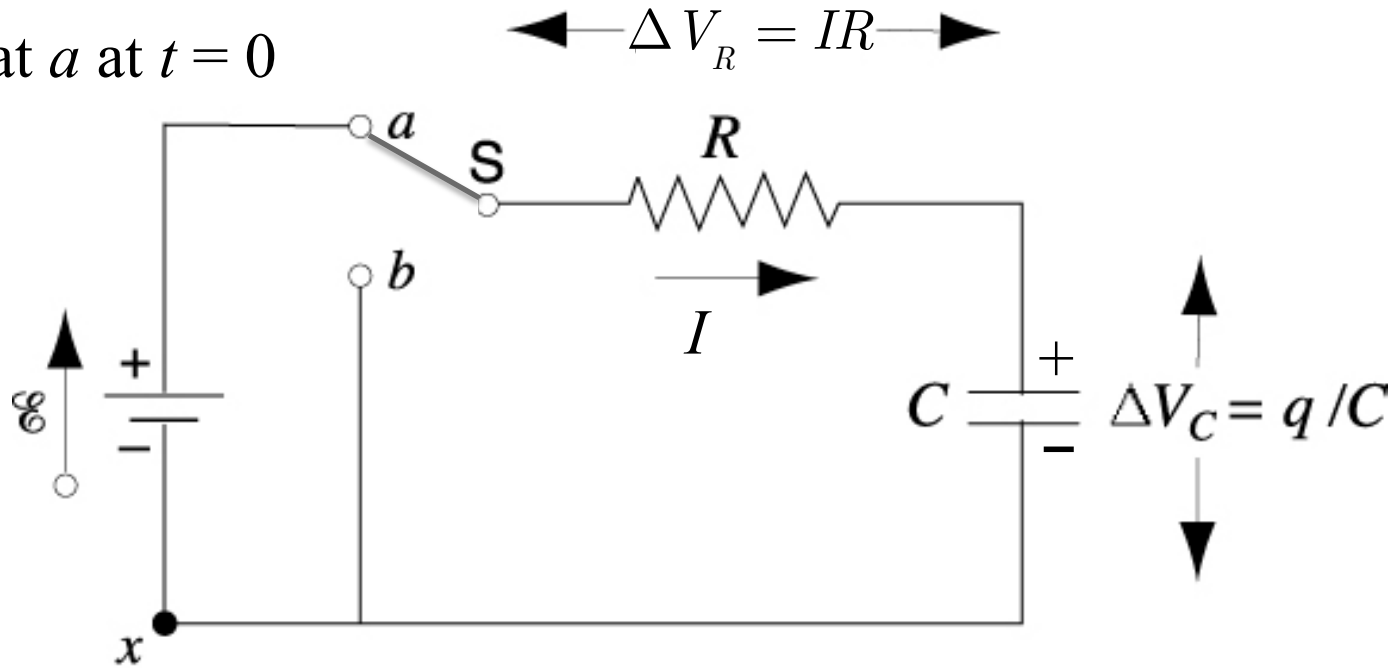



Kirchoff's 2nd law:
$$\varepsilon - IR - \frac{q}{C} = 0$$

$$\varepsilon = R \frac{dq}{dt} + \frac{q}{C}$$

$$q = C\varepsilon \left(1 - e^{-t/RC}\right)$$

$$I = \frac{\varepsilon}{R} e^{-t/RC}$$

RC circuits (charging a capacitor)

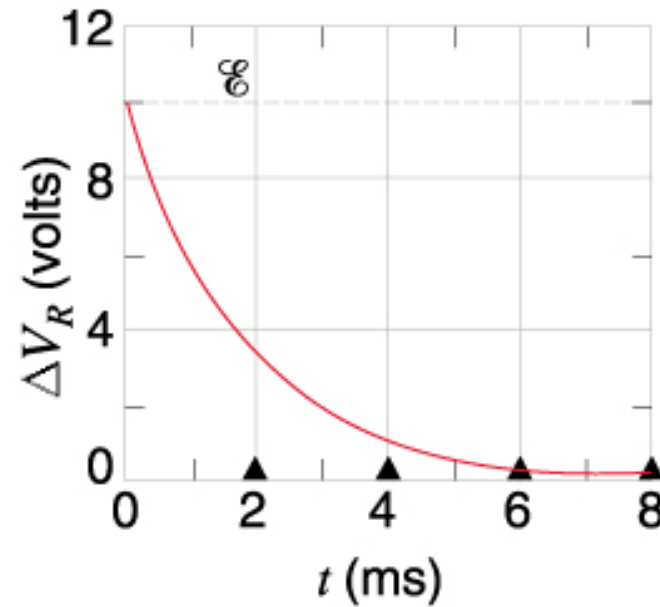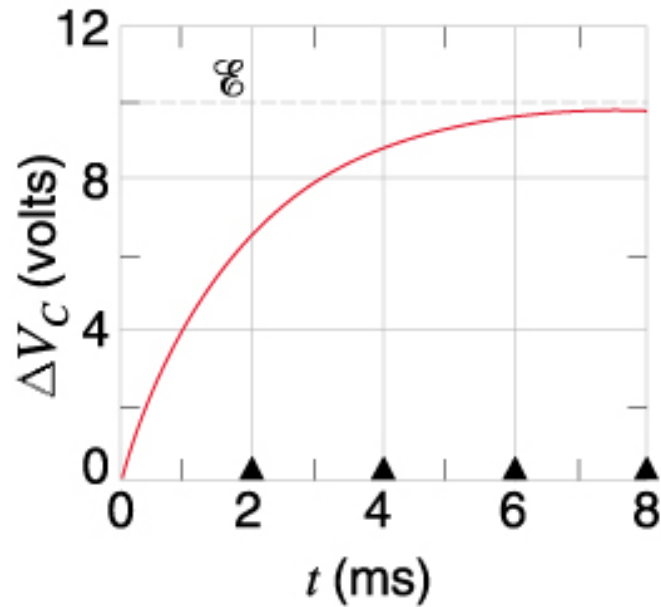

Kirchoff's 2nd law:
$$\mathcal{E} - IR - \frac{q}{C} = 0$$


$$\mathcal{E} = R \frac{dq}{dt} + \frac{q}{C}$$

$$q = C\mathcal{E} \left(1 - e^{-t/RC} \right)$$

$$I = \frac{\mathcal{E}}{R} e^{-t/RC}$$

RC circuits (discharging a capacitor)

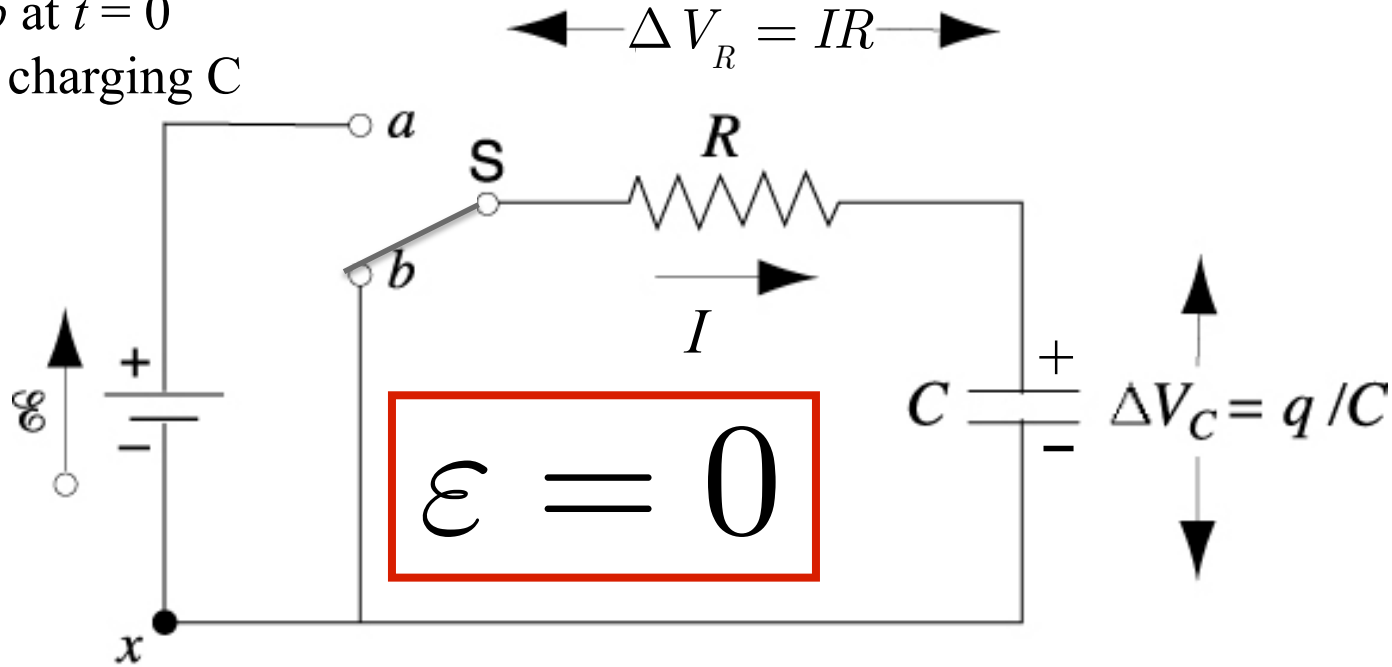Switch at b at $t = 0$
 After fully charging C




Kirchoff's 2nd law:
$$-IR - \frac{q}{C} = 0$$

$$q_0 = \varepsilon C \quad R \frac{dq}{dt} + \frac{q}{C} = 0$$

$$q = q_0 e^{-t/RC} \quad I = -\frac{q_0}{RC} e^{-t/RC} = -\frac{\varepsilon}{R} e^{-t/RC}$$

RC circuits (discharging a capacitor)

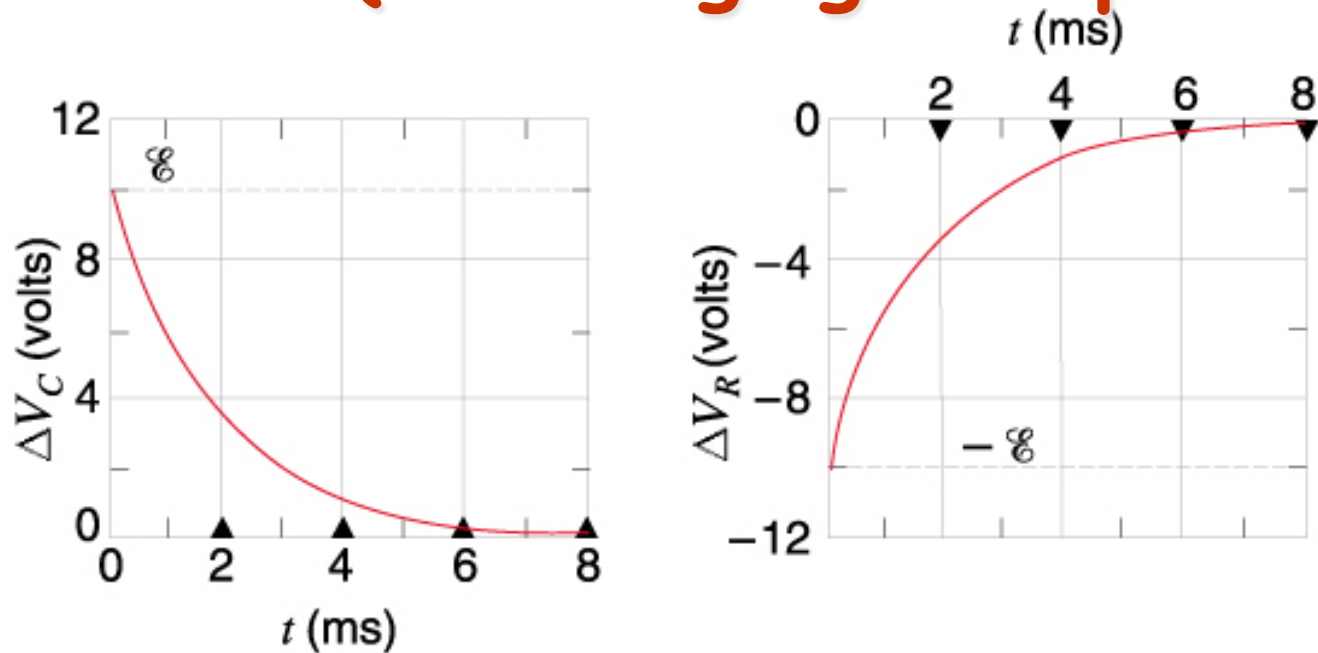

Kirchoff's 2nd law:

$$-IR - \frac{q}{C} = 0$$

$$q_0 = \varepsilon C$$

$$R \frac{dq}{dt} + \frac{q}{C} = 0$$

$$q = q_0 e^{-t/RC}$$

$$I = -\frac{q_0}{RC} e^{-t/RC} = -\frac{\varepsilon}{R} e^{-t/RC}$$