

Finish Chapter 27: Electromagnetic Induction

Chapter 28: Alternating-Current Circuits


Tuesday November 1st

- **Mini-exam 4 on Thursday**
 - Will cover Ch. 26 & 27 (LONCAPA 13-16)

- Review of Inductors
- Review of *RL* Circuits
- Energy and oscillations in *LC* circuits
- Intro to alternating current theory
 - Defⁿ of terms, e.g., rms values
 - Resistance
 - Capacitive reactance
 - Inductive reactance

Reading: up to page 498 in the text book (Ch. 28)

Review: Inductors

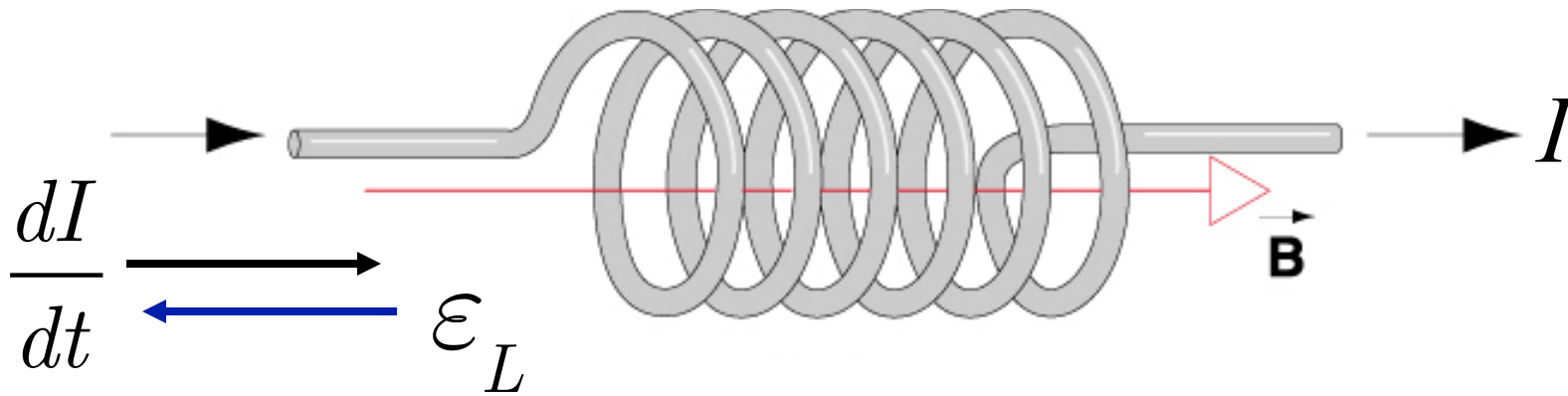

- We can, therefore, define a quantity L called inductance, which relates I to Φ_B and, thus, dI/dt and ε :

$$\Phi_B = LI$$

$$\varepsilon_L = -L \frac{dI}{dt}$$


Units for L :
weber/amp
T.m²/A
Henry (H)

Solenoid:


$$B = \mu_0 nI$$

$$L = \mu_0 n^2 Al$$

LR circuits (similarity to RC circuit)

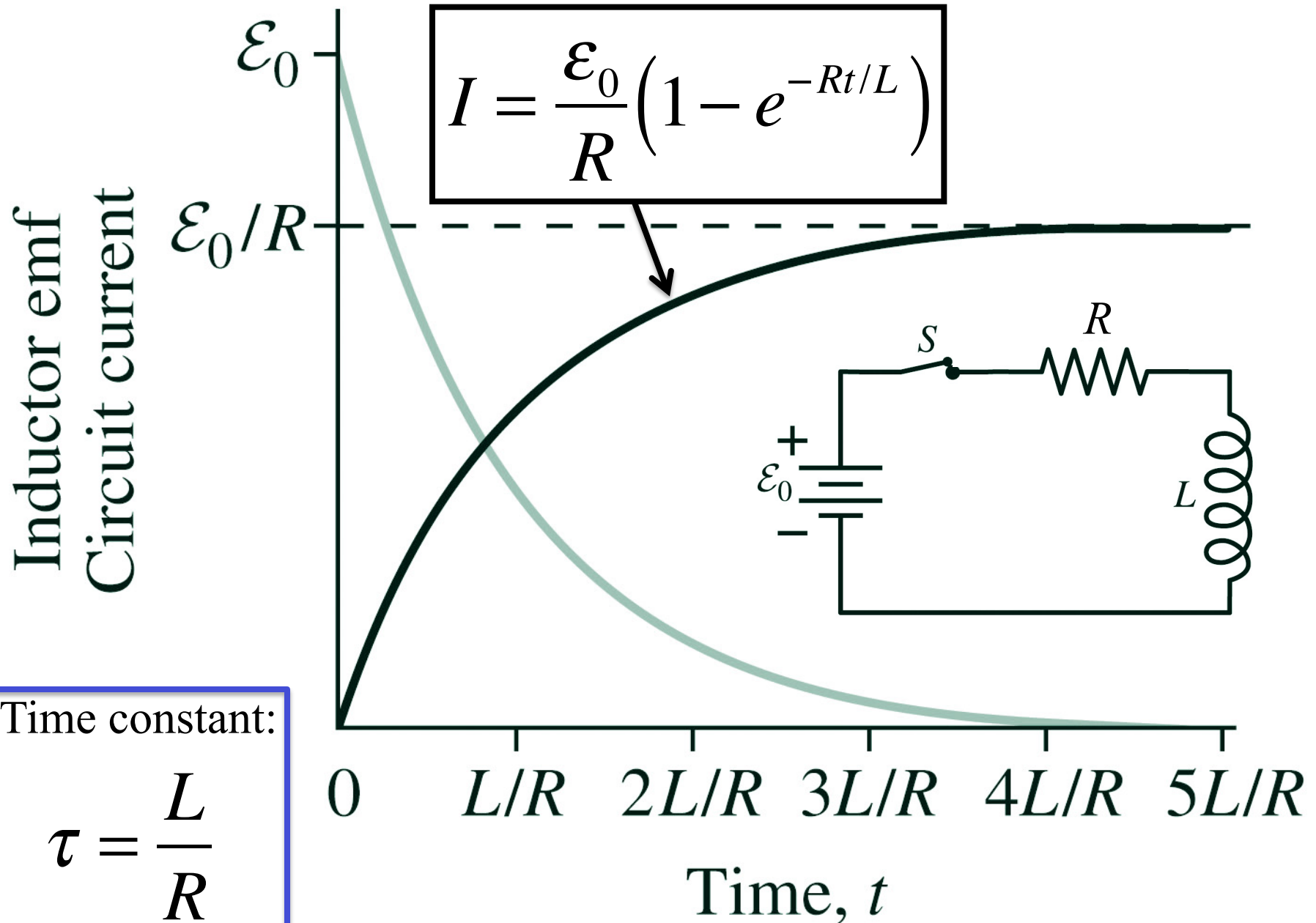


LR circuits (similarity to RC circuit)

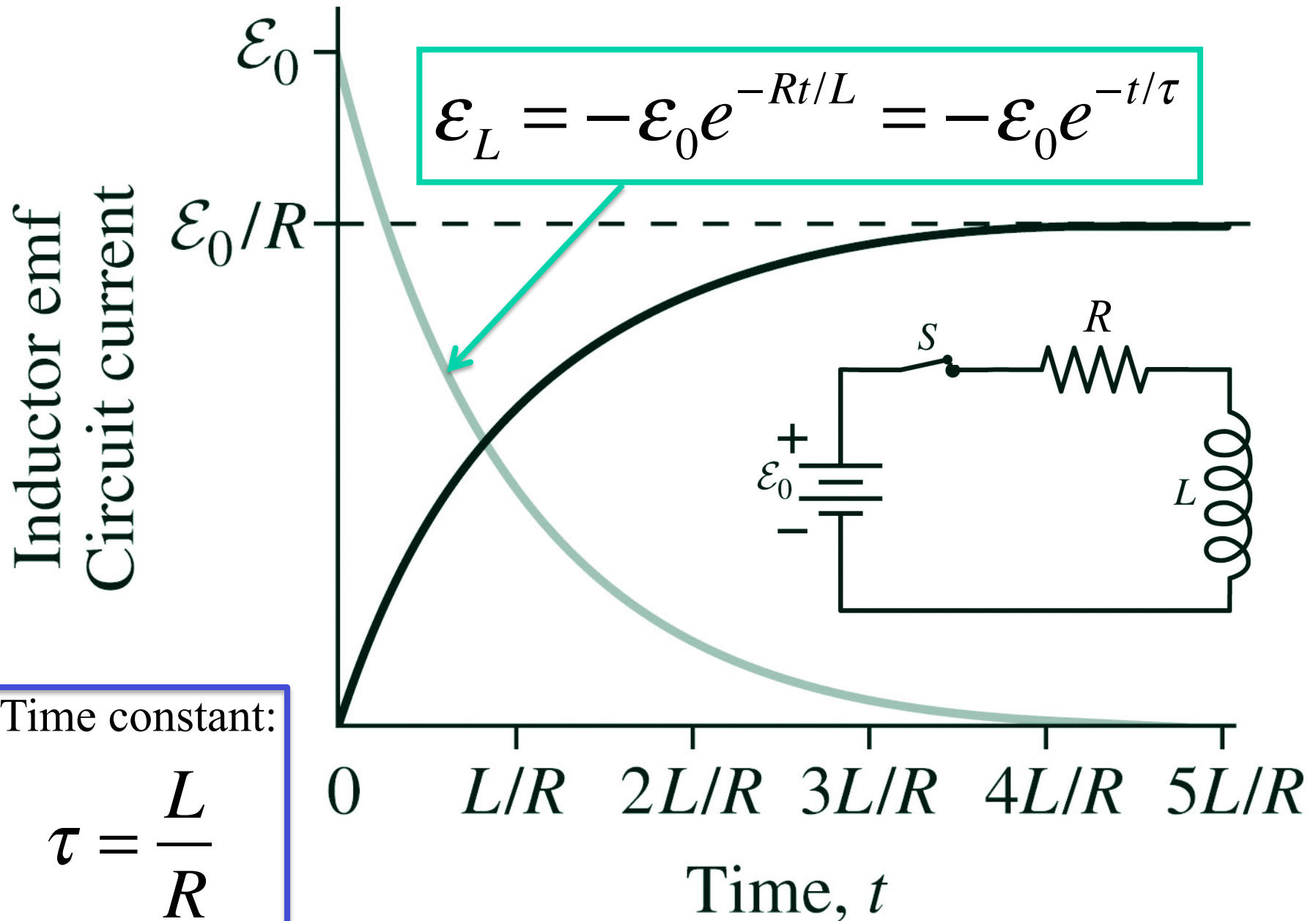

Time constant:

$$\tau = \frac{L}{R}$$

LR circuits (similarity to RC circuit)

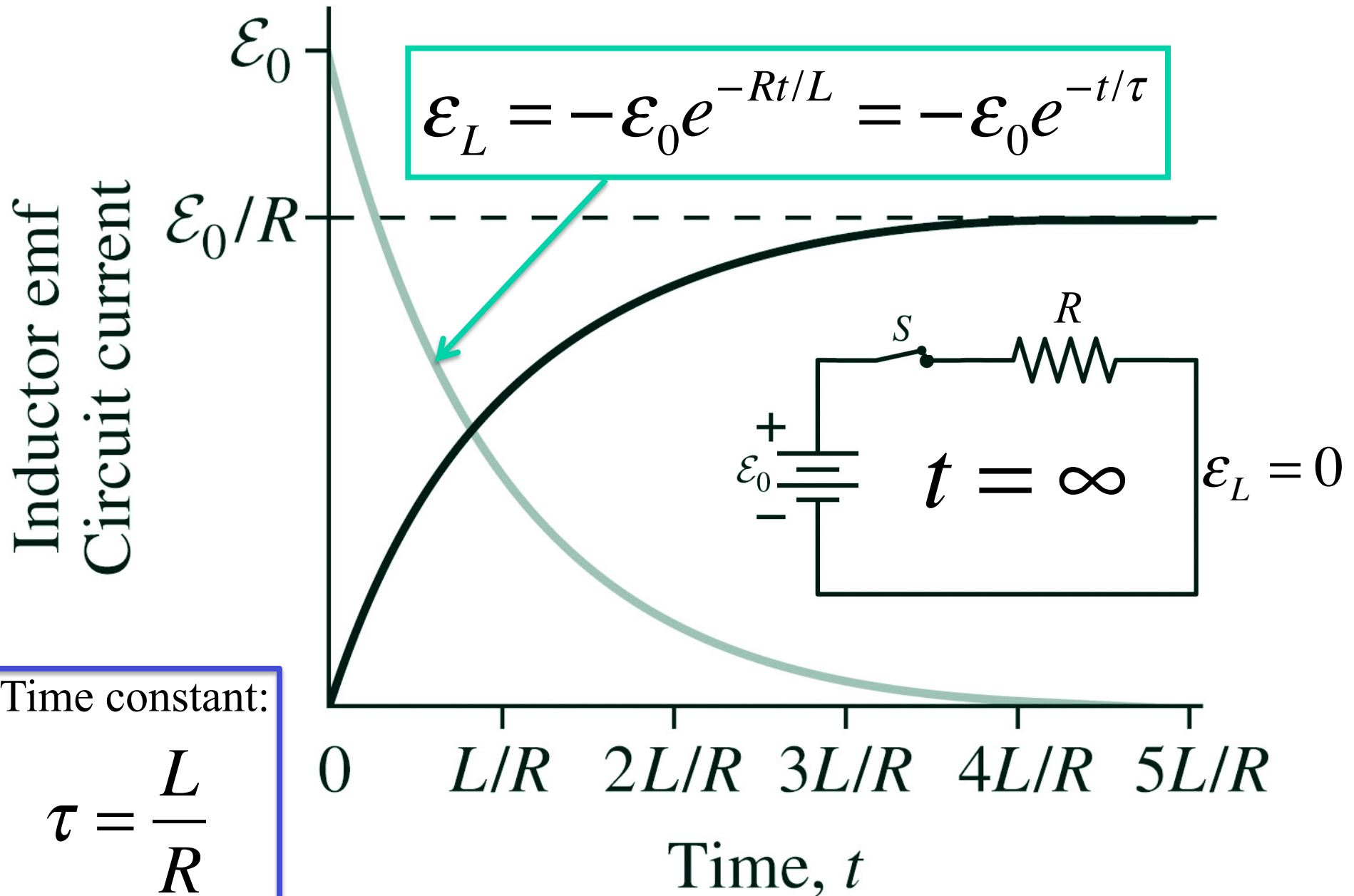


Time constant:

$$\tau = \frac{L}{R}$$

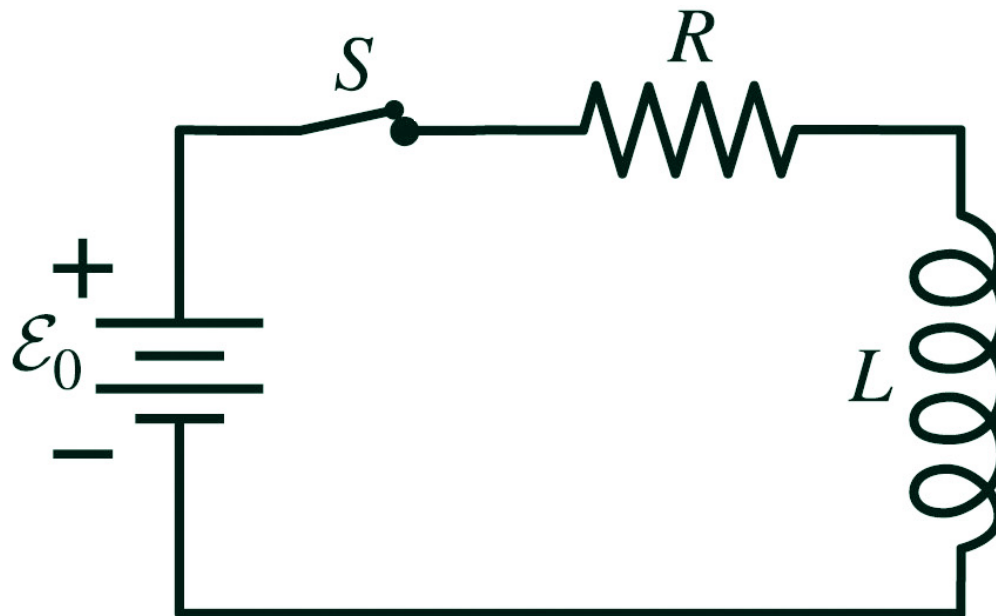
Example

A 3.5 V battery is connected in series with a switch, a resistor and an inductor. The switch is thrown at time $t = 0$. The current reaches half its maximum value after 1.2 ms. After a long time, the current reaches a maximum of 255 mA. Deduce values for the resistance and inductance in the circuit.



Energy Stored in an Inductor


Close switch
at time $t = 0$

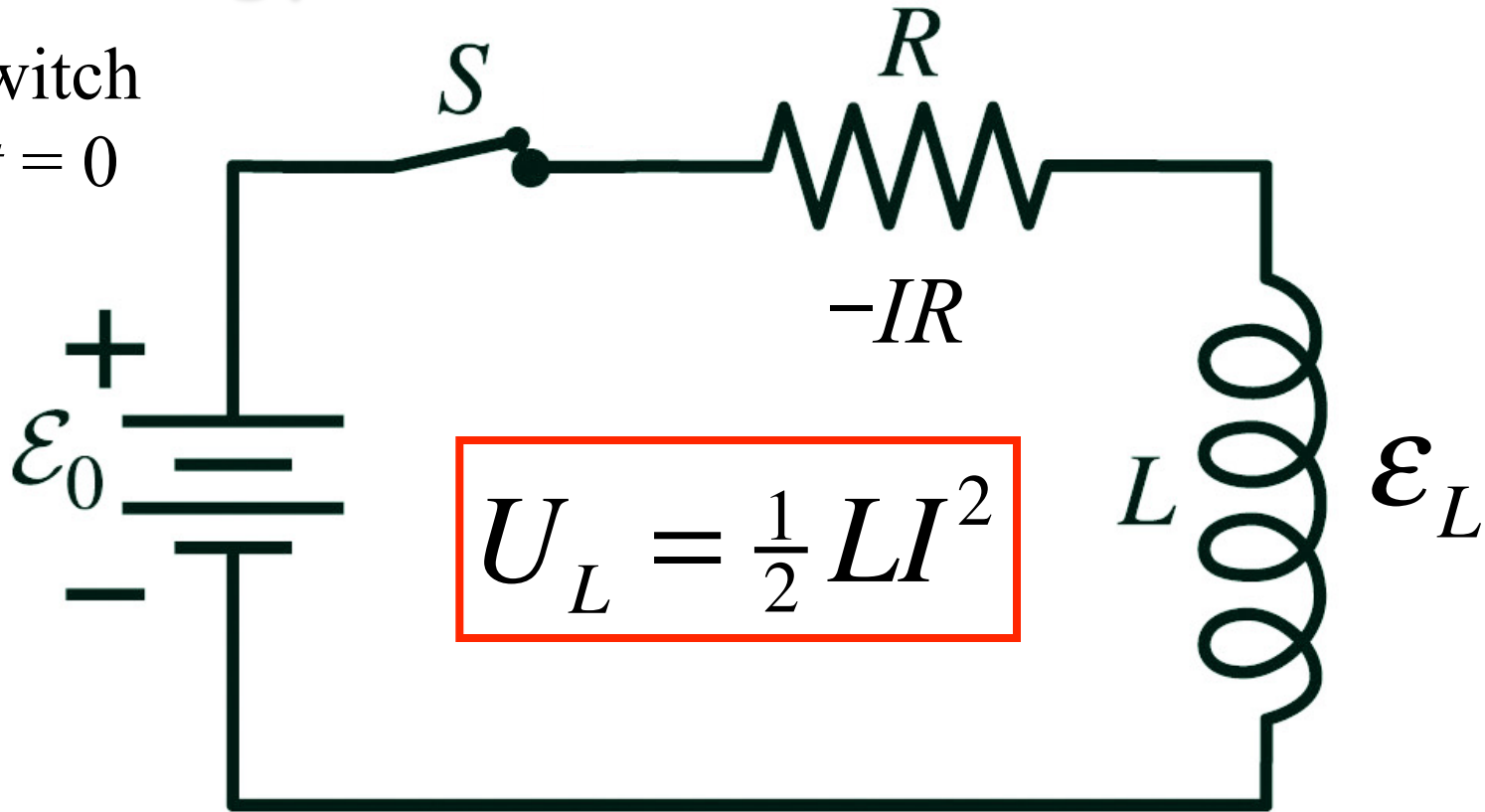

Energy stored in magnetic fields:


Energy density:
$$u_B = \frac{\text{Energy}}{\text{unit volume}} = \frac{B^2}{2\mu_0}$$

Ch. 28: Electromagnetic oscillations

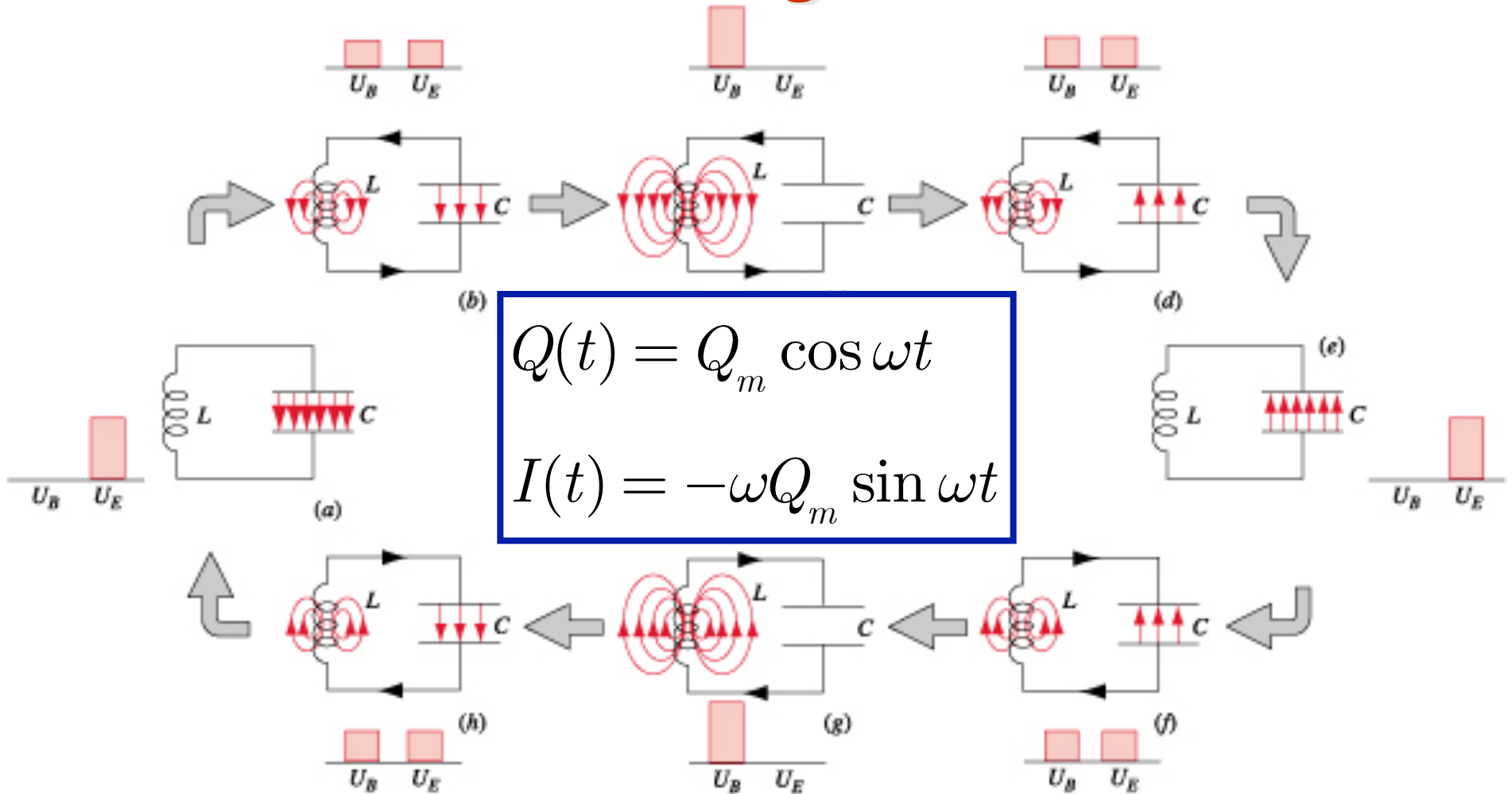

$$U = U_B + U_E = \frac{1}{2} LI^2 + \frac{1}{2} \frac{Q^2}{C}$$


Ch. 28: Electromagnetic oscillations

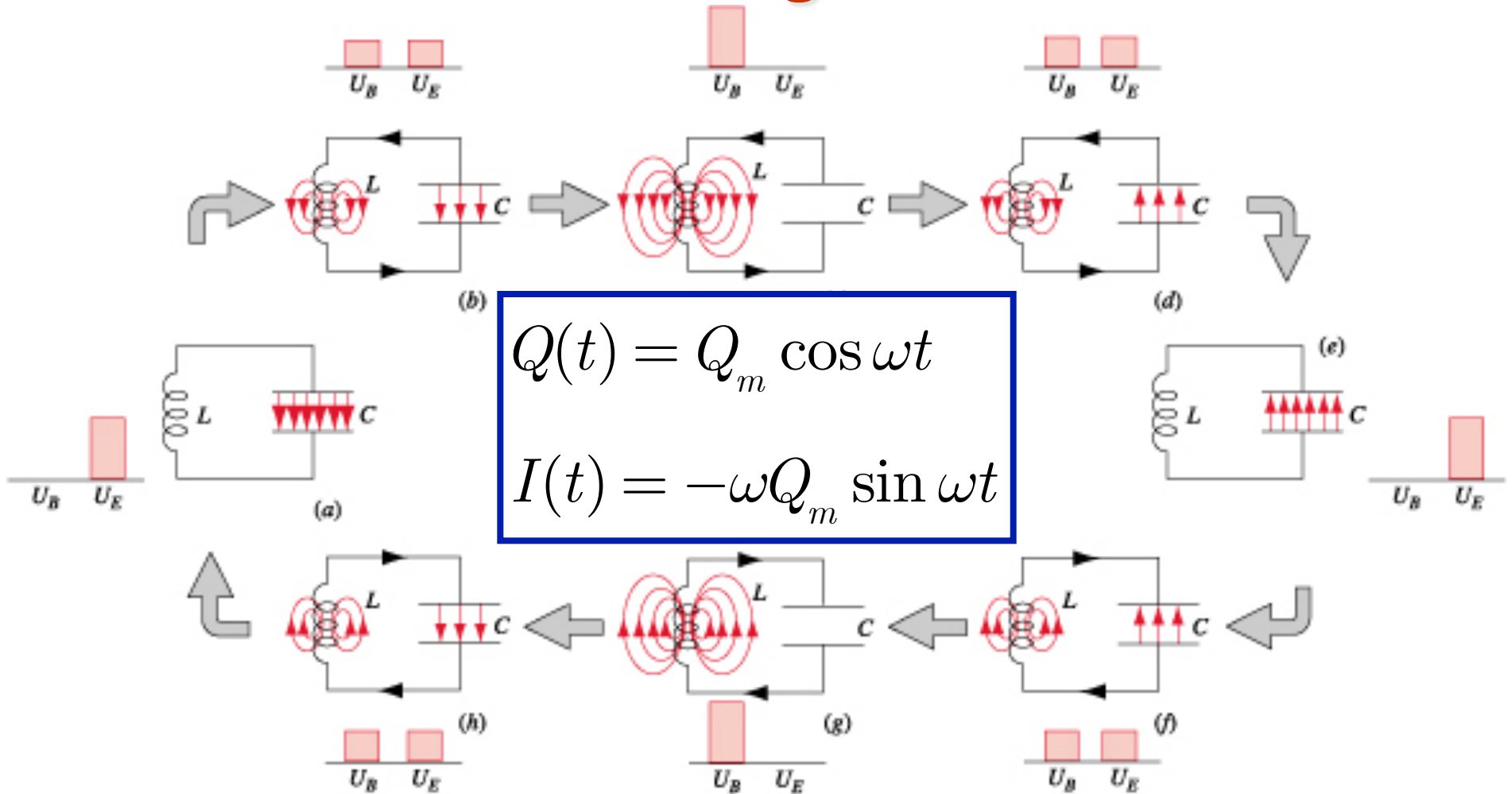

$$U = U_B + U_E = \frac{1}{2} LI^2 + \frac{1}{2} \frac{Q^2}{C}$$

$$\omega = \sqrt{\frac{1}{LC}}$$

Ch. 28: Electromagnetic oscillations

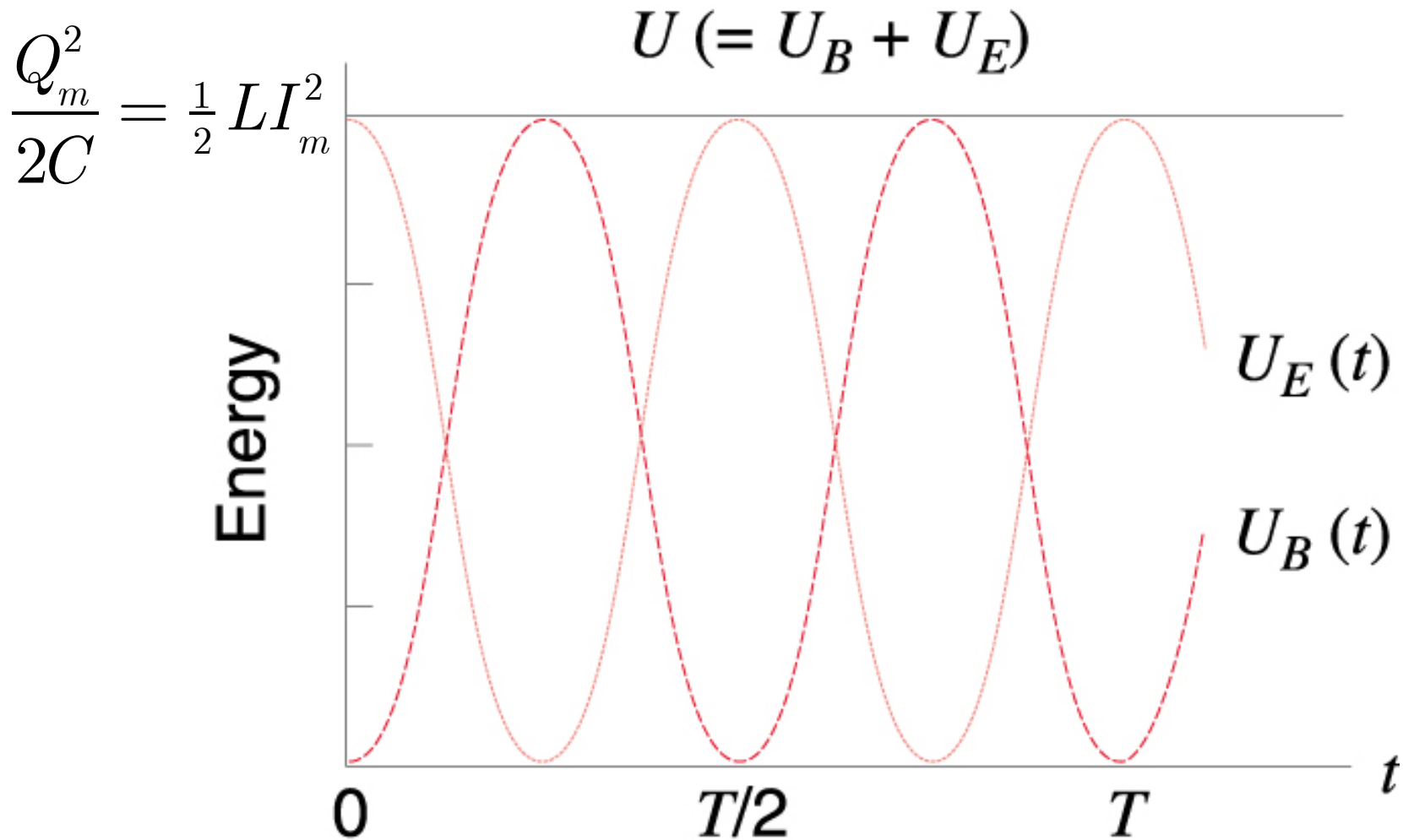

$$U = U_B + U_E = \frac{1}{2} LI^2 + \frac{1}{2} \frac{Q^2}{C}$$

Ch. 28: Alternating Current

$$V(t) = V_P \sin(\omega t + \phi_V); \quad I(t) = I_P \sin(\omega t + \phi_I)$$

Here
 $\omega t + \phi = 0$.

Voltage completes
a full cycle when
 ωt advances by 2π .

Angular frequency:

$$\omega = 2\pi f$$


In this example:

$$\phi_V = +\pi/6 \text{ or } 30^\circ$$

Root-Mean-Square:

$$V_{rms} = \frac{V_P}{\sqrt{2}}$$

$$I_{rms} = \frac{I_P}{\sqrt{2}}$$

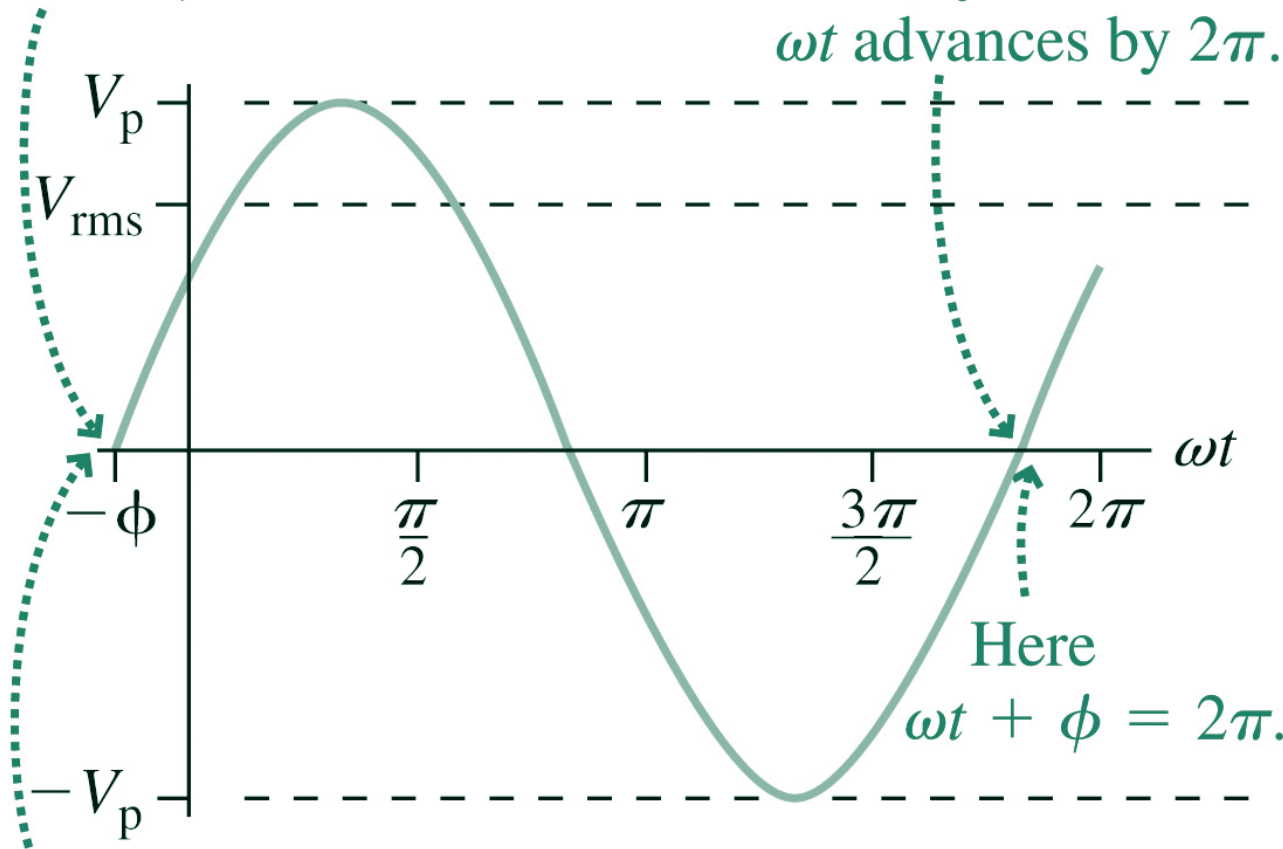

Sine curve starts at $\omega t = -\pi/6$ or -30°